

Module 2 DC Circuit

Lesson 3

Introduction of Electric Circuit

Objectives

- Familiarity with and understanding of the basic elements encountered in electric networks.
- To learn the fundamental differences between linear and nonlinear circuits.
- To understand the Kirchhoff's voltage and current laws and their applications to circuits.
- Meaning of circuit ground and the voltages referenced to ground.
- Understanding the basic principles of voltage dividers and current dividers.
- Potentiometer and loading effects.
- To understand the fundamental differences between ideal and practical voltage and current sources and their mathematical models to represent these source models in electric circuits.
- Distinguish between independent and dependent sources those encountered in electric circuits.
- Meaning of delivering and absorbing power by the source.

L.3.1 Introduction

The interconnection of various electric elements in a prescribed manner comprises as an electric circuit in order to perform a desired function. The electric elements include controlled and uncontrolled source of energy, resistors, capacitors, inductors, etc. Analysis of electric circuits refers to computations required to determine the unknown quantities such as voltage, current and power associated with one or more elements in the circuit. To contribute to the solution of engineering problems one must acquire the basic knowledge of electric circuit analysis and laws. Many other systems, like mechanical, hydraulic, thermal, magnetic and power system are easy to analyze and model by a circuit. To learn how to analyze the models of these systems, first one needs to learn the techniques of circuit analysis. We shall discuss briefly some of the basic circuit elements and the laws that will help us to develop the background of subject.

L-3.1.1 Basic Elements & Introductory Concepts


Electrical Network: A combination of various electric elements (Resistor, Inductor, Capacitor, Voltage source, Current source) connected in any manner what so ever is called an electrical network. We may classify circuit elements in two categories, passive and active elements.

Passive Element: The element which receives energy (or absorbs energy) and then either converts it into heat (R) or stored it in an electric (C) or magnetic (L) field is called passive element.


Active Element: The elements that supply energy to the circuit is called active element. Examples of active elements include voltage and current sources, generators, and electronic devices that require power supplies. A transistor is an active circuit element, meaning that it can amplify power of a signal. On the other hand, transformer is not an active element because it does not amplify the power level and power remains same both

in primary and secondary sides. Transformer is an example of passive element.

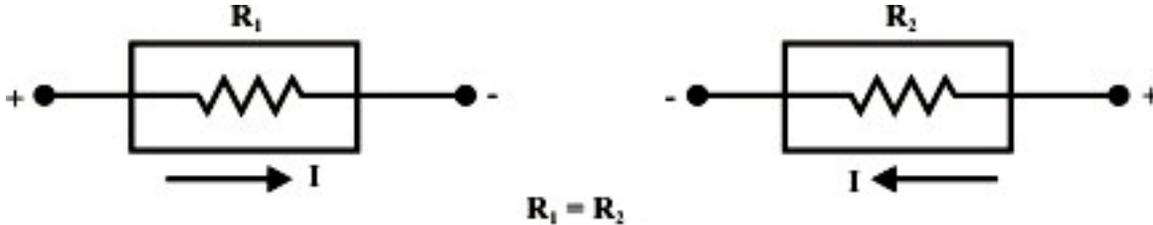Bilateral Element: Conduction of current in both directions in an element (example: Resistance; Inductance; Capacitance) with same magnitude is termed as bilateral element.



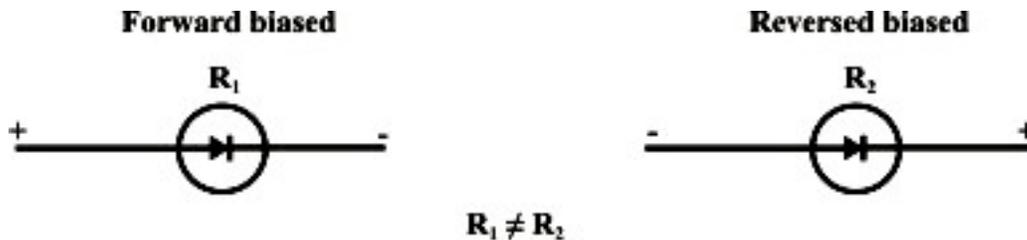Unilateral Element: Conduction of current in one direction is termed as unilateral (example: Diode, Transistor) element.



Meaning of Response: An application of input signal to the system will produce an output signal, the behavior of output signal with time is known as the response of the system.

L-3.2 Linear and Nonlinear Circuits

Linear Circuit: Roughly speaking, a linear circuit is one whose parameters do not change with voltage or current. More specifically, a linear system is one that satisfies (i) homogeneity property [response of $\alpha u(t)$ equals α times the response of $u(t)$, $S(\alpha u(t)) = \alpha S(u(t))$ for all α ; and $u(t)$] (ii) additive property [that is the response of system due to an input $(\alpha_1 u_1(t) + \alpha_2 u_2(t))$ equals the sum of the response of input $\alpha_1 u_1(t)$ and the response of input $\alpha_2 u_2(t)$, $S(\alpha_1 u_1(t) + \alpha_2 u_2(t)) = \alpha_1 S(u_1(t)) + \alpha_2 S(u_2(t))$.] When an input $u_1(t)$ or $u_2(t)$ is applied to a system “ S ”, the corresponding output response of the system is observed as $S(u_1(t)) = y_1(t)$ or $S(u_2(t)) = y_2(t)$ respectively. Fig. 3.1 explains the meaning of homogeneity and additive properties of a system.

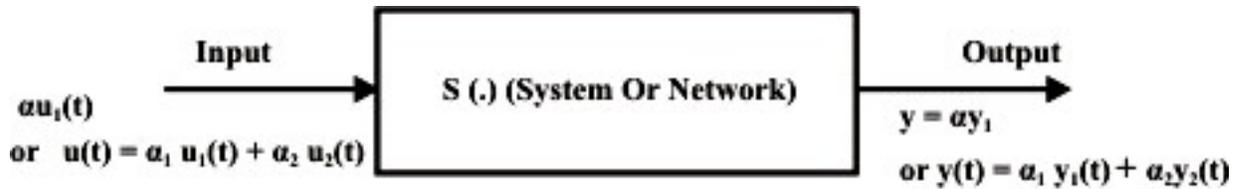


Fig. 3.1: Input output behavior of a system

Non-Linear Circuit: Roughly speaking, a non-linear system is that whose parameters change with voltage or current. More specifically, non-linear circuit does not obey the homogeneity and additive properties. Volt-ampere characteristics of linear and non-linear elements are shown in figs. 3.2 - 3.3. In fact, a circuit is linear if and only if its input and output can be related by a straight line passing through the origin as shown in fig.3.2. Otherwise, it is a nonlinear system.

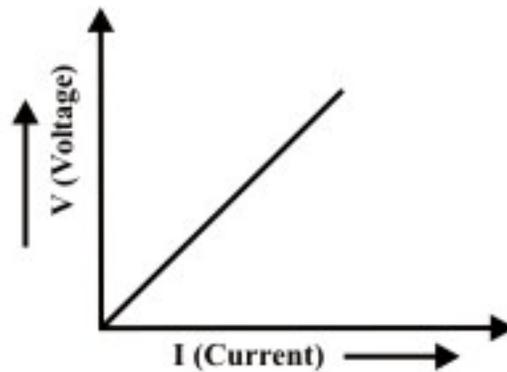


Fig. 3.2: V-I characteristics of linear element.

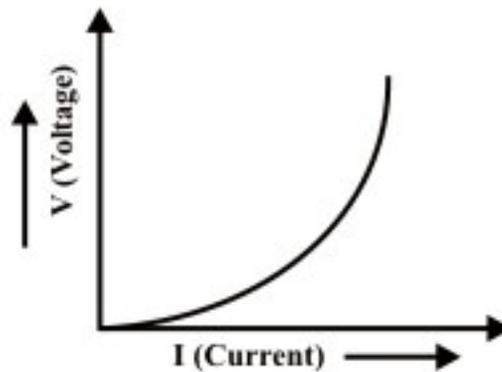


Fig. 3.3: V-I characteristics of non-linear element.

Potential Energy Difference: The voltage or potential energy difference between two points in an electric circuit is the amount of energy required to move a unit charge between the two points.

L-3.3 Kirchhoff's Laws

Kirchhoff's laws are basic analytical tools in order to obtain the solutions of currents and voltages for any electric circuit; whether it is supplied from a direct-current system or an alternating current system. But with complex circuits the equations connecting the currents and voltages may become so numerous that much tedious algebraic work is involved in their solutions.

Elements that generally encounter in an electric circuit can be interconnected in various possible ways. Before discussing the basic analytical tools that determine the currents and voltages at different parts of the circuit, some basic definition of the following terms are considered.

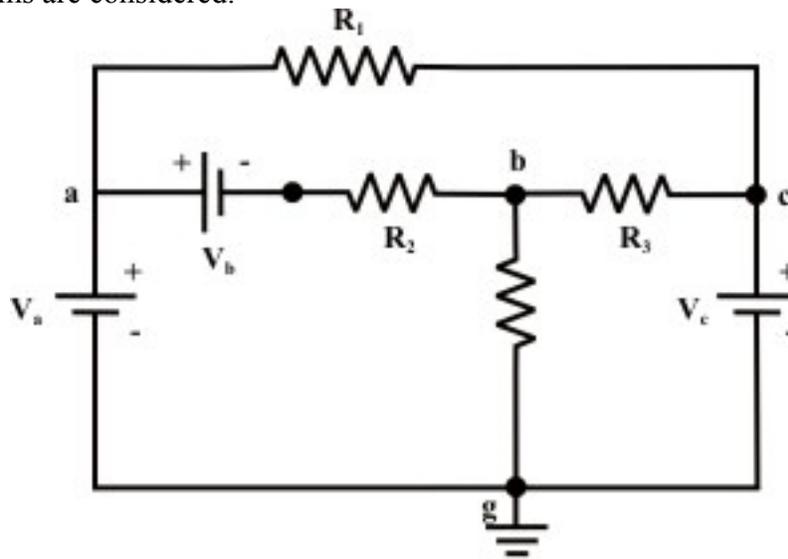


Fig. 3.4: A simple resistive network

- Node- A node in an electric circuit is a point where two or more components are connected together. This point is usually marked with dark circle or dot. The circuit in fig. 3.4 has nodes a, b, c, and g. Generally, a point, or a node in an circuit specifies a certain voltage level with respect to a reference point or node.
- Branch- A branch is a conducting path between two nodes in a circuit containing the electric elements. These elements could be sources, resistances, or other elements. Fig.3.4 shows that the circuit has six branches: three resistive branches (a-c, b-c, and b-g) and three branches containing voltage and current sources (a-, a-, and c-g).
- Loop- A loop is any closed path in an electric circuit i.e., a closed path or loop in a circuit is a contiguous sequence of branches which starting and end points for tracing the path are, in effect, the same node and touches no other node more than once. Fig. 3.4 shows three loops or closed paths namely, a-b-g-a; b-c-g-b; and a-c-b-a. Further, it may be noted that the outside closed paths a-c-g-a and a-b-c-g-a are also form two loops.
- Mesh- a mesh is a special case of loop that does not have any other loops within it or in its interior. Fig. 3.4 indicates that the first three loops (a-b-g-a; b-c-g-b; and a-c-b-a) just identified are also 'meshes' but other two loops (a-c-g-a and a-b-c-g-

a) are not.

With the introduction of the Kirchhoff's laws, a various types of electric circuits can be analyzed.

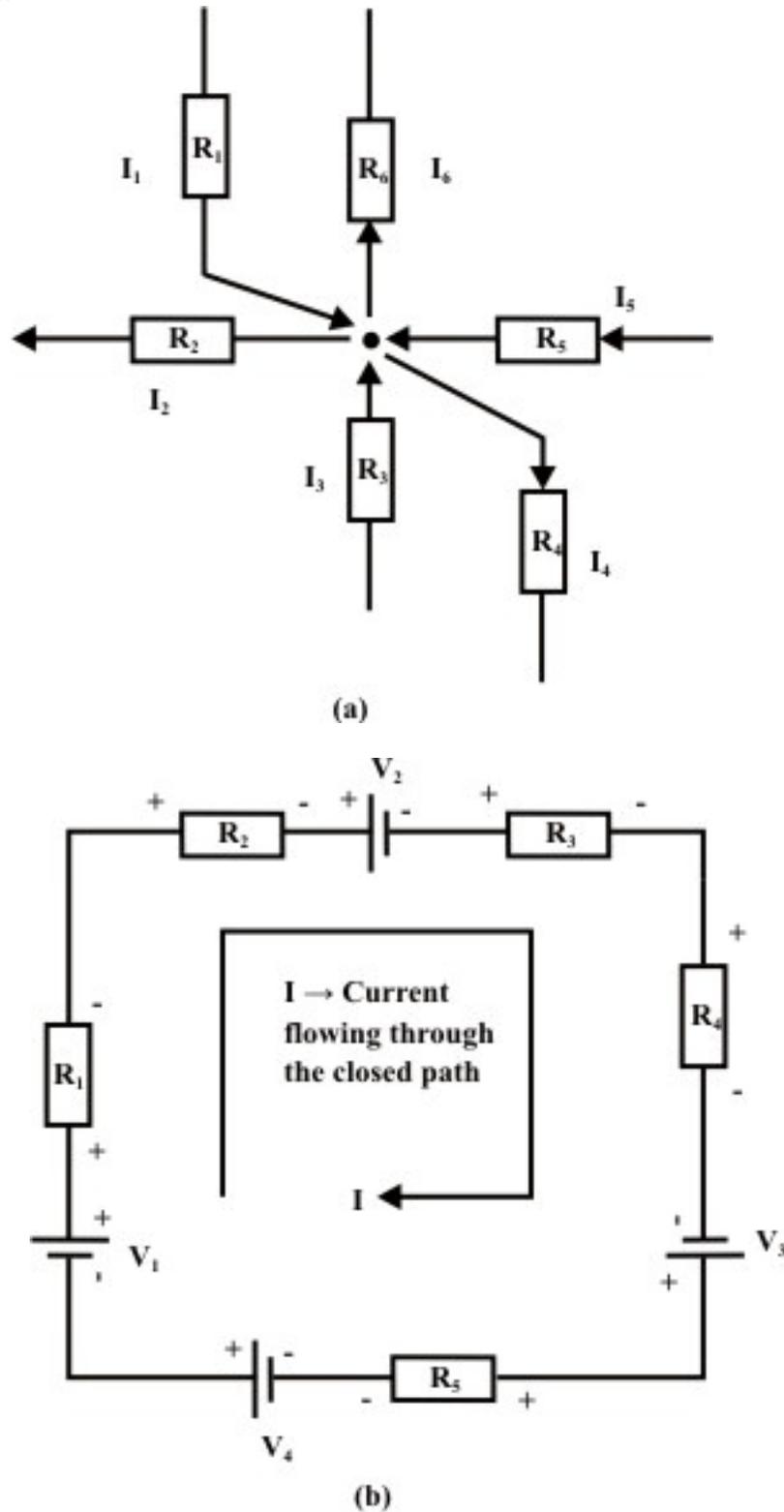


Fig. 3.5: Illustrates the Kirchhoff's laws

Kirchhoff's Current Law (KCL): KCL states that at any node (junction) in a circuit the algebraic sum of currents entering and leaving a node at any instant of time must be equal to zero. Here currents entering(+ve sign) and currents leaving (-ve sign) the node must be assigned opposite algebraic signs (see fig. 3.5 (a), $I_1 - I_2 + I_3 - I_4 + I_5 - I_6 = 0$).

Kirchhoff's Voltage Law (KVL): It states that in a closed circuit, the algebraic sum of all source voltages must be equal to the algebraic sum of all the voltage drops. Voltage drop is encountered when current flows in an element (resistance or load) from the higher-potential terminal toward the lower potential terminal. Voltage rise is encountered when current flows in an element (voltage source) from lower potential terminal (or negative terminal of voltage source) toward the higher potential terminal (or positive terminal of voltage source). Kirchhoff's voltage law is explained with the help of fig. 3.5(b).

KVL equation for the circuit shown in fig. 3.5(b) is expressed as (we walk in clockwise direction starting from the voltage source V_1 and return to the same point)

$$V_1 - IR_1 - IR_2 - V_2 - IR_3 - IR_4 + V_3 - IR_5 - V_4 = 0$$

$$V_1 - V_2 + V_3 - V_4 = IR_1 + IR_2 + IR_3 + IR_4 + IR_5$$

Example: L-3.1 For the circuit shown in fig. 3.6, calculate the potential of points A, B, C, and E with respect to point D. Find also the value of voltage source V_1 .

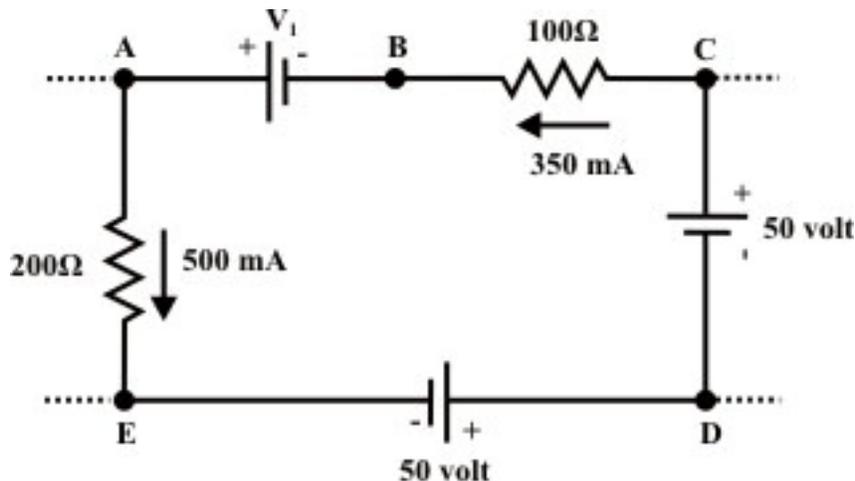


Fig. 3.6: A part of dc resistive circuit is presented

Solution Let us assume we move in clockwise direction around the close path D-E-A-B-C-D and stated the following points.

- 50 volt source is connected between the terminals D & E and this indicates that the point E is lower potential than D. So, V_{ED} (i.e., it means potential of E with respect to D) is -50 volt and similarly $V_{CD} = 50 \text{ volt}$ or $V_{DC} = -50 \text{ volt}$.
- 500 mA current is flowing through 200Ω resistor from A to E and this implies that point A is higher potential than E. If we move from lower potential (E) to

higher potential (A), this shows there is a rise in potential. Naturally, $V_{AE} = 500 \times 10^{-3} \times 200 = 100 \text{ volt}$ and $V_{AD} = -50 + 100 = 50 \text{ volt}$. Similarly, $V_{CB} = 350 \times 10^{-3} \times 100 = 35 \text{ volt}$

- V_1 voltage source is connected between A & B and this indicates that the terminal B is lower potential than A i.e., $V_{AB} = V_1 \text{ volt}$ or $V_{BA} = -V_1 \text{ volt}$. One can write the voltage of point B with respect to D is $V_{BD} = 50 - V_1 \text{ volt}$.

- One can write *KVL* law around the closed-loop D-E-A-B-C-D as $V_{ED} + V_{AE} + V_{BA} + V_{CB} + V_{DC} = 0$
 $-50 + 100 - V_1 + 35 - 50 = 0 \Rightarrow V_1 = 35 \text{ volt}$.

Now we have $V_{ED} = -50 \text{ volt}$, $V_{AD} = -50 + 100 = 50 \text{ volt}$, $V_{BD} = 50 - 35 = 15 \text{ volt}$,
 $V_{CD} = 15 + 35 = 50 \text{ volt}$.

L-3.4 Meaning of Circuit Ground and the Voltages referenced to Ground

In electric or electronic circuits, usually maintain a reference voltage that is named “ground voltage” to which all voltages are referred. This reference voltage is thus at ground potential or zero potential and each other terminal voltage is measured with respect to ground potential, some terminals in the circuit will have voltages above it (positive) and some terminals in the circuit will have voltages below it (negative) or in other words, some potential above or below ground potential or zero potential.

Consider the circuit as shown in fig. 3.7 and the common point of connection of elements V_1 & V_3 is selected as ground (or reference) node. When the voltages at different nodes are referred to this ground (or reference) point, we denote them with double subscripted voltages V_{ED} , V_{AD} , V_{BD} , and V_{CD} . Since the point D is selected as ground potential or zero potential, we can write V_{ED} as V_E , V_{AD} as V_A and so on.

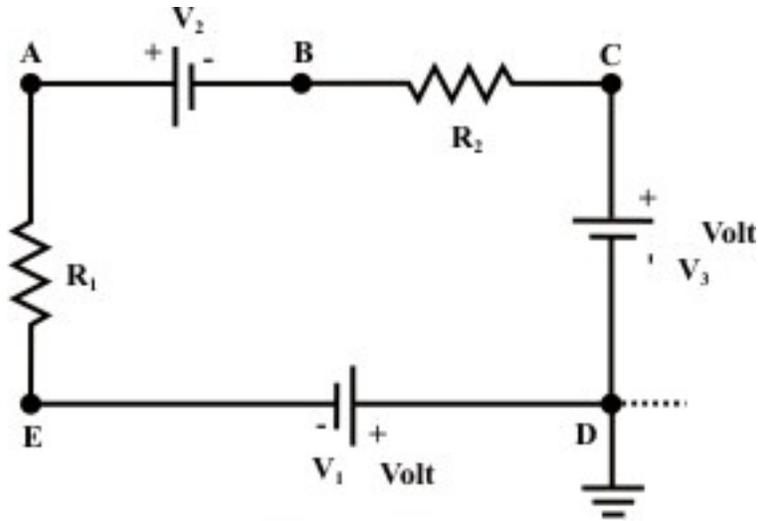


Fig. 3.7: A Simple dc resistive circuit

In many cases, such as in electronic circuits, the chassis is shorted to the earth itself for safety reasons.

L-3.5 Understanding the Basic Principles of Voltage Dividers and Current dividers

L-3.5.1 Voltage Divider

Very often, it is useful to think of a series circuit as a voltage divider. The basic idea behind the voltage divider is to assign a portion of the total voltage to each resistor. In Figure 3.8 (a), suppose that the source voltage is E . By the circuit configuration shown one can divide off any voltage desired (V_{out}), less than the supply voltage E , by adjusting R_1 , R_2 and R_3 .

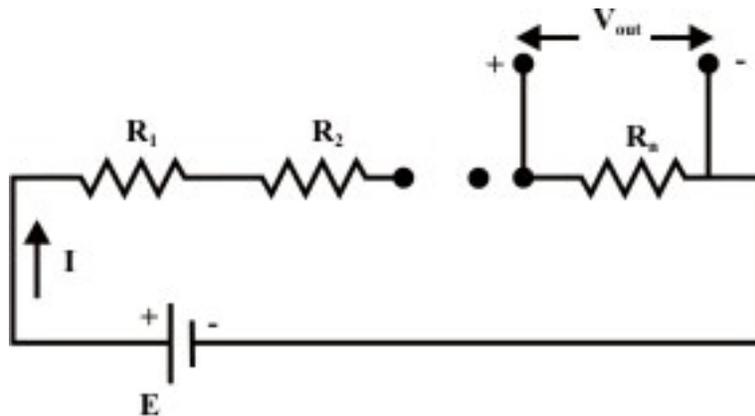


Fig. 3.8(a): Voltage Divider

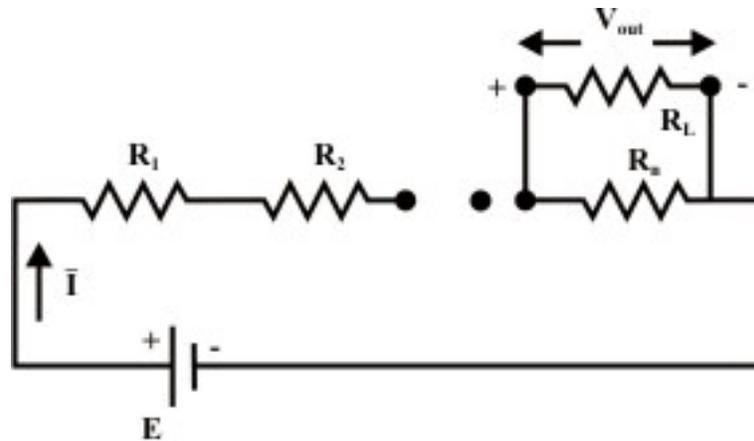


Fig. 3.8(b): Voltage Divider With Load

From figure 3.8(a) the output of the voltage divider V_{out} is computed by the relation

$$V_{out} = I R_n = \frac{E}{R_1 + R_2 + \dots + R_n} R_n \quad (3.1)$$

Equation (3.1) indicates that the voltage across any resistor R_i ($R_i, i=1,2,\dots,n$) in a series circuit is equal to the applied voltage (E) across the circuit multiplied by a factor

$\frac{R_i}{\sum_{j=1}^n R_j}$. It should be noted that this expression is only valid if the same current

I flows through all the resistors. If a load resistor R_L is connected to the voltage divider (see figure 3.8(b)), one can easily modify the expression (3.1) by simply combining R_L & R_n in parallel to find a new \bar{R}_n and replacing R_n by \bar{R}_n in equation (3.1).

Example: L-3.2 For the circuit shown in Figure 3.9,

- (i) Calculate V_{out} , ignoring the internal resistance R_s of the source E . Use voltage division.
- (ii) Recalculate V_{out} taking into account the internal resistance R_s of the source. What percent error was introduced by ignoring R_s in part (i)?

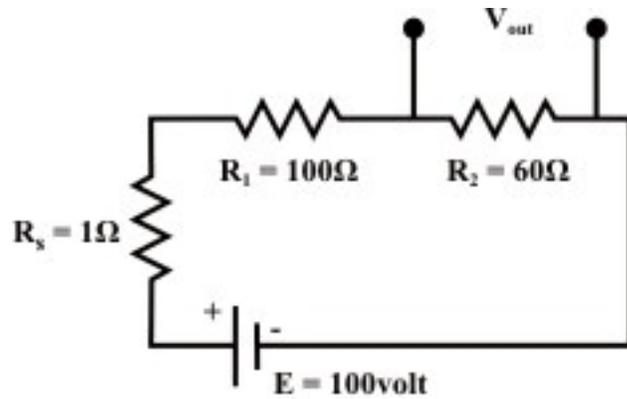


Fig. 3.9

Solution: Part (i): From equation (3.1) the output voltage V_{out} across the resistor $R_2 = \frac{E}{R_1 + R_2} R_2 = \frac{100}{100 + 60} \times 60 = 37.9 \text{ volt}$ (when the internal resistance R_s of the source is considered zero.) Similarly, $V_{out} = 37.27 \text{ volt}$ when R_s is taken into account for calculation. Percentage error is computed as $= \frac{37.9 - 37.27}{37.27} \times 100 = 1.69\%$

L-3.5.2 Current divider

Another frequently encountered in electric circuit is the current divider. Figure 3.10 shows that the current divider divides the source current I_s between the two resistors.

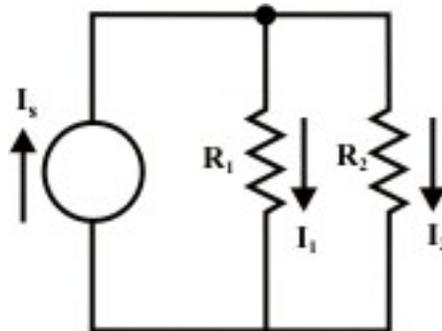


Fig. 3.10: Current Divider

The parallel combination of two resistors is sometimes termed as current divider, because the supply current is distributed between the two branches of the circuit. For the circuit, assume that the voltage across the branch is V and the current expression in R_1 resistor can be written as

$$\frac{I_1}{I_s} = \frac{\frac{V}{R_1}}{V\left(\frac{1}{R_1} + \frac{1}{R_2}\right)} = \frac{R_2}{R_1 + R_2} \text{ or } I_1 = \frac{R_2}{R_1 + R_2} \times I_s. \text{ Similarly, the current flowing through}$$

the R_2 can be obtained as $I_2 = \frac{R_1}{R_1 + R_2} \times I_s$. It can be noted that the expression for I_1 has R_2 on its top line, that for I_2 has R_1 on its top line.

Example: L-3.3 Determine I_1, I_2, I_3 & I_5 using only current divider formula when $I_4 = 4A$.

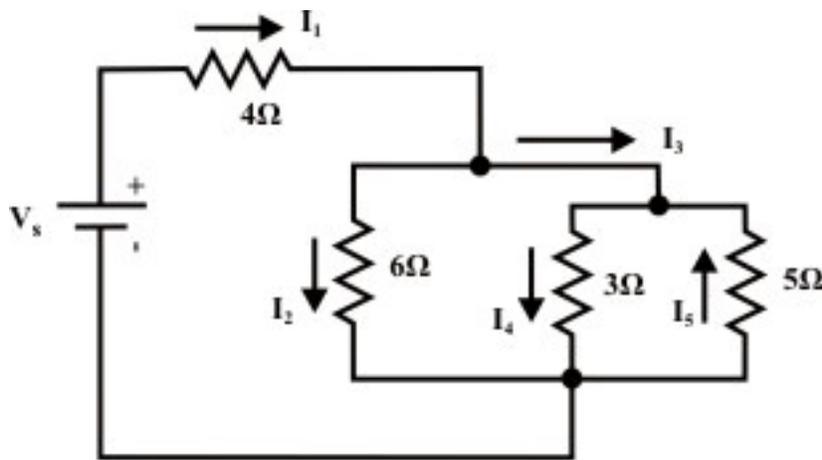


Fig. 3.11

Solution- Using the current division formula we can write $I_4 = \frac{5}{5+3} I_3 = \frac{5}{8} I_3 \rightarrow I_3 = \frac{4 \times 8}{5} = 6.4 A$. Similarly, $-I_5 = \frac{3}{8} \times I_3 \rightarrow I_5 = \frac{3}{8} \times 6.4 = 2.4 A$.

Furthermore, we can write $I_3 = \frac{6}{6+(3\parallel 5)} I_1 = \frac{6}{6+1.879} I_1 \rightarrow I_1 = \frac{7.879}{6} \times 6.4 = 8.404 A$ and

$$I_2 = \frac{1.879}{6+1.879} \times I_1 = 2.004 A.$$

L-3.6 Potentiometer and its function

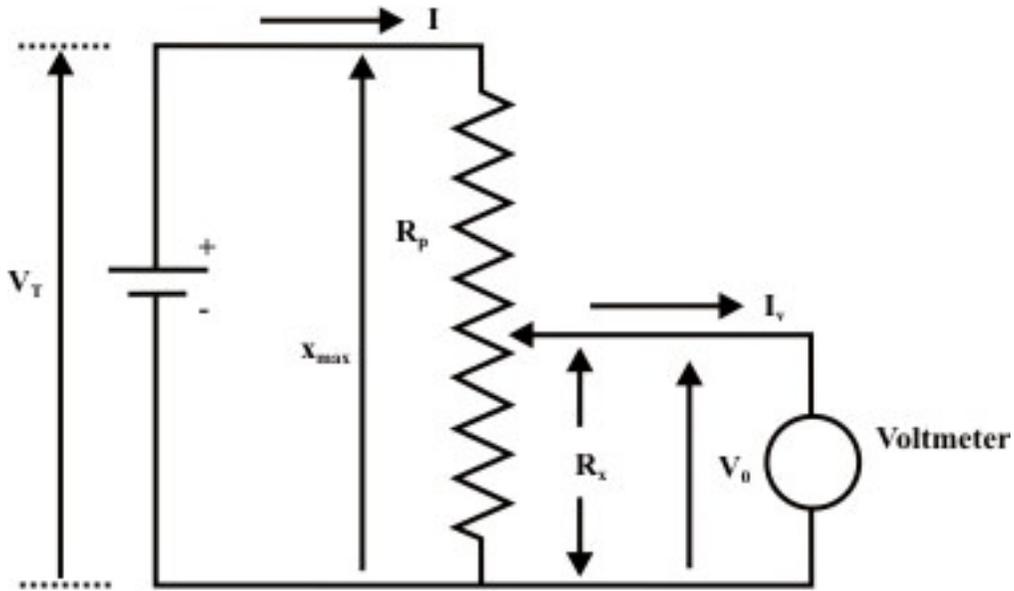


Fig. 3.12: A voltmeter is connected across the output terminals of potentiometer

The potentiometer has a resistance R_p and its wiper can move from top position $x = x_{\max}$ to bottom position $x = 0$. The resistance R_x corresponds to the position x of the wiper such that

$$\frac{R_x}{x} = \frac{R_p}{x_{\max}} \Rightarrow R_x = \left(\frac{R_p}{x_{\max}} \right) x \quad (\text{assumed that the per unit length resistance of the}$$

potentiometer is same through out its length). Figure 3.12 represents a potentiometer whose output is connected to a voltmeter. In true sense, the measurement of the output voltage V_o with a voltmeter is affected by the voltmeter resistance R_v and the relationship between V_o and x ($x =$ wiper distance from the bottom position) can easily be established. We know that the voltmeter resistance is very high in $M \Omega$ range and practically negligible current is flowing through the voltmeter. Under this condition, one can write the expression for voltage between the wiper and the bottom end terminal of the potentiometer as

$$V_{out} (= I R_x) = \frac{V_T (= I R_p)}{x_{\max}} \times x \Rightarrow V_{out} = V_T \times \frac{x}{x_{\max}} = V_{out} = V_T \times \frac{R_x}{R_p}$$

It may be noted that depending on the position of movable tap terminal the output voltage (V_{out}) can be controlled. By adjusting the wiper toward the top terminal, we can increase V_{out} . The opposite effect can be observed while the movable tap moves toward the bottom terminal. A simple application of potentiometer in real practice is the volume control of a radio receiver by adjusting the applied voltage to the input of audio amplifier

of a radio set. This audio amplifier boosts this voltage by a certain fixed factor and this voltage is capable of driving the loudspeaker.

Example- L-3.4 A $500\text{-k}\Omega$ potentiometer has 110 V applied across it. Adjust the position of R_{bot} such that 47.5 V appears between the movable tap and the bottom end terminal (refer fig.3.12).

Solution- Since the output voltage (V_{bot}) is not connected to any load, in turn, we can write the following expression

$$V_{out} = V_T \times \frac{x}{x_{max}} \frac{V_{bot}}{V_T} = \frac{R_{bot}}{R_T} \rightarrow R_{bot} = \frac{V_{bot}}{V_T} \times R_T = \frac{47.5}{110} \times 500000 = 216\text{-k}\Omega.$$

L-3.7 Practical Voltage and Current Sources

L-3.7.1 Ideal and Practical Voltage Sources

- An ideal voltage source, which is represented by a model in fig.3.13, is a device that produces a constant voltage across its terminals ($V = E$) no matter what current is drawn from it (terminal voltage is independent of load (resistance) connected across the terminals)

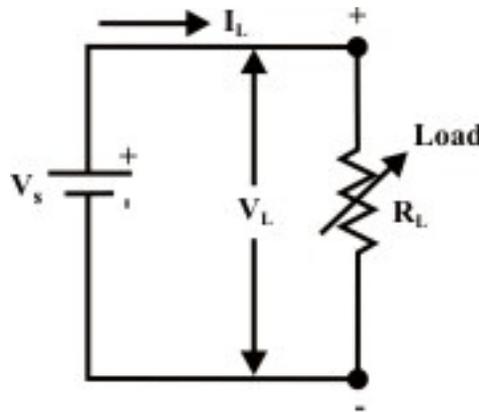


Fig. 3.13: Ideal dc voltage source

For the circuit shown in fig.3.13, the upper terminal of load is marked plus (+) and its lower terminal is marked minus (-). This indicates that electrical potential of upper terminal is V_L volts higher than that of lower terminal. The current flowing through the load R_L is given by the expression $V_s = V_L = I_L R_L$ and we can represent the terminal $V-I$ characteristic of an ideal dc voltage as a straight line parallel to the x-axis. This means that the terminal voltage V_L remains constant and equal to the source voltage V_s irrespective of load current is small or large. The $V-I$ characteristic of ideal voltage source is presented in Figure 3.14.

- However, real or practical dc voltage sources do not exhibit such characteristics (see fig. 3.14) in practice. We observed that as the load resistance R_L connected across the source is decreased, the corresponding load current I_L increases while the terminal voltage across the source decreases (see eq.3.1). We can realize such voltage drop across the terminals with increase in load current provided a resistance element (R_s) present inside the voltage source. Fig. 3.15 shows the model of practical or real voltage source of value V_s .

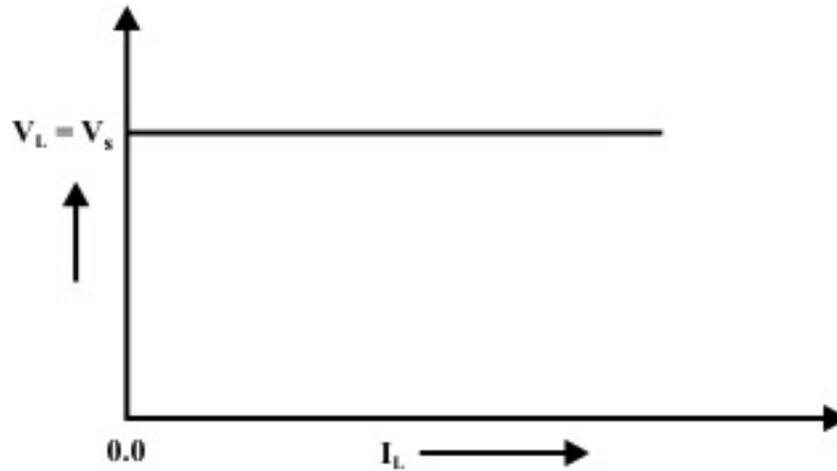


Fig. 3.14: V-I characteristics of ideal voltage source

The terminal $V - I$ characteristics of the practical voltage source can be described by an equation

$$V_L = V_s - I_L R_s \quad (3.1)$$

and this equation is represented graphically as shown in fig.3.16. In practice, when a load resistance R_L more than 100 times larger than the source resistance R_s , the source can be considered approximately ideal voltage source. In other words, the internal resistance of the source can be omitted. This statement can be verified using the relation $R_L = 100R_s$ in equation (3.1). The practical voltage source is characterized by two parameters namely known as (i) Open circuit voltage (V_s) (ii) Internal resistance in the source's circuit model. In many practical situations, it is quite important to determine the source parameters experimentally. We shall discuss briefly a method in order to obtain source parameters.

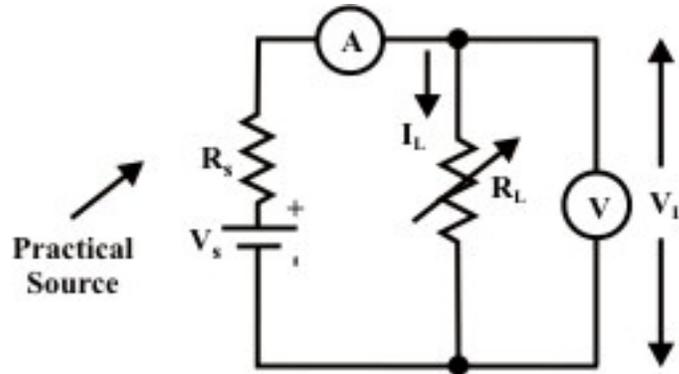


Fig. 3.15: Practical dc voltage source model

Method:- Connect a variable load resistance across the source terminals (see fig. 3.15). A voltmeter is connected across the load and an ammeter is connected in series with the load resistance. Voltmeter and Ammeter readings for several choices of load resistances are presented on the graph paper (see fig. 3.16). The slope of the line is $-R_s$, while the curve intercepts with voltage axis (at $I_L = 0$) is the value of V_s .

The $V-I$ characteristic of the source is also called the source's **“regulation curve” or “load line”**. The open-circuit voltage is also called the “no-load” voltage, V_{oc} . The maximum allowable load current (rated current) is known as full-load current I_{FL} and the corresponding source or load terminal voltage is known as “full-load” voltage V_{FL} . We know that the source terminal voltage varies as the load is varied and this is due to internal voltage drop inside the source. The percentage change in source terminal voltage from no-load to full-load current is termed the “voltage regulation” of the source. It is defined as

$$\text{Voltage regulation (\%)} = \frac{V_{oc} - V_{FL}}{V_{FL}} \times 100$$

For ideal voltage source, there should be no change in terminal voltage from no-load to full-load and this corresponds to “zero voltage regulation”. For best possible performance, the voltage source should have the lowest possible regulation and this indicates a smallest possible internal voltage drop and the smallest possible internal resistance.

Example:-L-3.5 A practical voltage source whose short-circuit current is 1.0A and open-circuit voltage is 24 Volts. What is the voltage across, and the value of power dissipated in the load resistance when this source is delivering current 0.25A?

Solution: From fig. 3.10, $I_{sc} = \frac{V_s}{R_s} = 1.0A$ (short-circuit test) $V_{oc} = V_s = 24 \text{ volts}$ (open-circuit test). Therefore, the value of internal source resistance is obtained as $R_s = \frac{V_s}{I_{sc}} = 24\Omega$. Let us assume that the source is delivering current $I_L = 0.25A$ when the

load resistance R_L is connected across the source terminals. Mathematically, we can write the following expression to obtain the load resistance R_L .

$$\frac{24}{24 + R_L} = 0.25 \rightarrow R_L = 72 \Omega.$$

Now, the voltage across the load $R_L = I_L R_L = 0.25 \times 72 = 18 \text{ volts.}$, and the power consumed by the load is given by $P_L = I_L^2 R_L = 0.0625 \times 72 = 4.5 \text{ watts.}$

Example-L-3.6 (Refer fig. 3.15) A certain voltage source has a terminal voltage of 50 V when $I = 400 \text{ mA}$; when I rises to its full-load current value 800 mA the output voltage is recorded as 40 V. Calculate (i) Internal resistance of the voltage source (R_s). (ii) No-load voltage (open circuit voltage V_s). (iii) The voltage Regulation.

Solution- From equation (3.1) ($V_L = V_s - I_L R_s$) one can write the following expressions under different loading conditions.

$50 = V_s - 0.4 R_s$ & $40 = V_s - 0.8 R_s \rightarrow$ solving these equations we get, $V_s = 60V$ & $R_s = 25 \Omega$.

$$\text{Voltage regulation (\%)} = \frac{V_{oc} - V_{FL}}{V_{FL}} \times 100 = \frac{60 - 40}{40} \times 100 = 50\%$$

L-3.7.2 Ideal and Practical Current Sources

- Another two-terminal element of common use in circuit modeling is 'current source' as depicted in fig.3.17. An ideal current source, which is represented by a model in fig. 3.17(a), is a device that delivers a constant current to any load resistance connected across it, no matter what the terminal voltage is developed across the load (i.e., independent of the voltage across its terminals across the terminals).

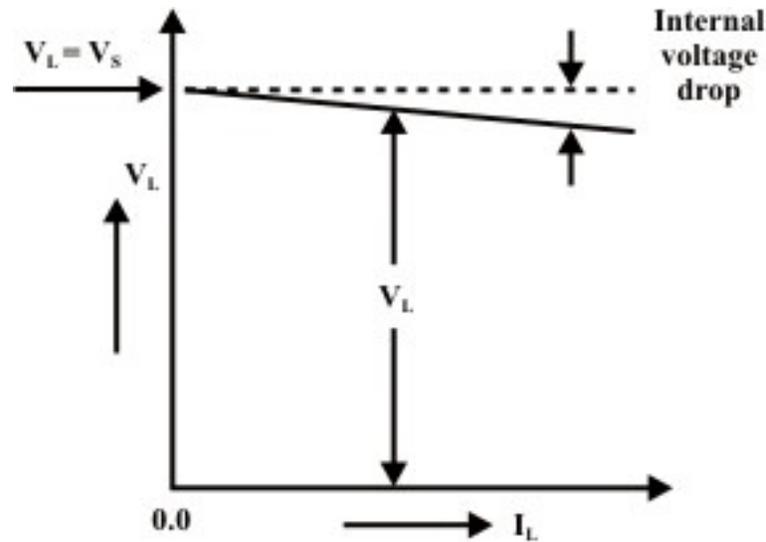


Fig. 3.16: V-I characteristics of practical voltage source

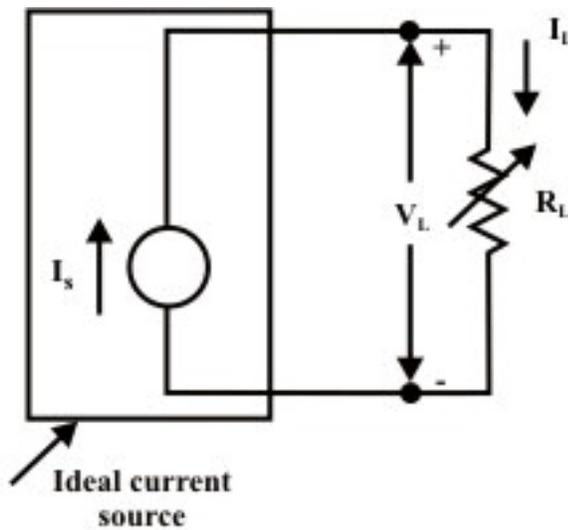


Fig. 3.17(a): Ideal current source with variable load

It can be noted from model of the current source that the current flowing from the source to the load is always constant for any load resistance (see fig. 3.19(a)) i.e. whether R_L is small (V_L is small) or R_L is large (V_L is large). The vertical dashed line in fig. 3.18 represents the $V-I$ characteristic of ideal current source. In practice, when a load R_L is connected across a practical current source, one can observe that the current flowing in load resistance is reduced as the voltage across the current source's terminal is increased, by increasing the load resistance R_L . Since the distribution of source current in two parallel paths entirely depends on the value of external resistance that connected across the source (current source) terminals. This fact can be realized by introducing a parallel resistance R_s in parallel with the practical current source I_s , as shown in fig. 3.17(b). The dark lines in fig. 3.18 show

the $V - I$ characteristic (load-line) of practical current source. The slope of the curve represents the internal resistance of the source. One can apply KCL at the top terminal of the current source in fig. 3.17(b) to obtain the following expression.

$$I_L = I_s - \frac{V_L}{R_s} \text{ Or } V_L = I_s R_s - R_s I_L = V_{oc} - R_s I_L \quad (3.2)$$

The open circuit voltage and the short-circuit current of the practical current source are given by $V_{oc} = I_s R_s$ and $I_{short} = I_s$ respectively. It can be noted from the fig.3.18 that source 1 has a larger internal resistance than source 2 and the slope the curve indicates the internal resistance R_s of the current source. Thus, source 1 is closer to the ideal source. More specifically, if the source internal resistance $R_s \geq 100 R_L$ then source acts nearly as an ideal current source.

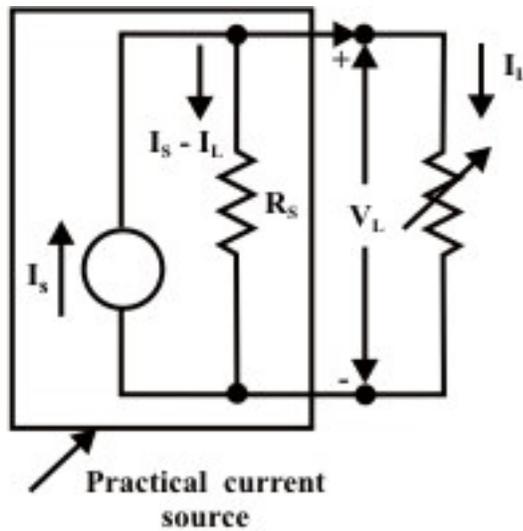


Fig. 3.17(b): Practical current source with variable load

L-3.7.3 Conversion of a Practical Voltage Source to a Practical Current source and vice-versa

- Voltage Source to Current Source

For the practical voltage source in fig. 3.19(a), the load current is calculated as

$$I_L = \frac{V_s}{R_s + R_L} \quad (3.3)$$

Note that the maximum current delivered by the source when $R_L = 0$ (under short-circuit condition) is given by $I_{max} = I_s = \frac{V_s}{R_s}$. From eq.(3.3) one can rewrite the expression for load current as

$$I_L = \frac{I_s \times R_s}{R_s + R_L} \quad (3.4)$$

A simple current divider circuit having two parallel branches as shown in fig.3.19 (b) can realize by the equation (3.4).

Note: A practical voltage source with a voltage V_s and an internal source resistance R_s can be replaced by an equivalent practical current source with a current $I_s = \frac{V_s}{R_s}$ and a source internal resistance R_s (see fig. 3.19(b)).

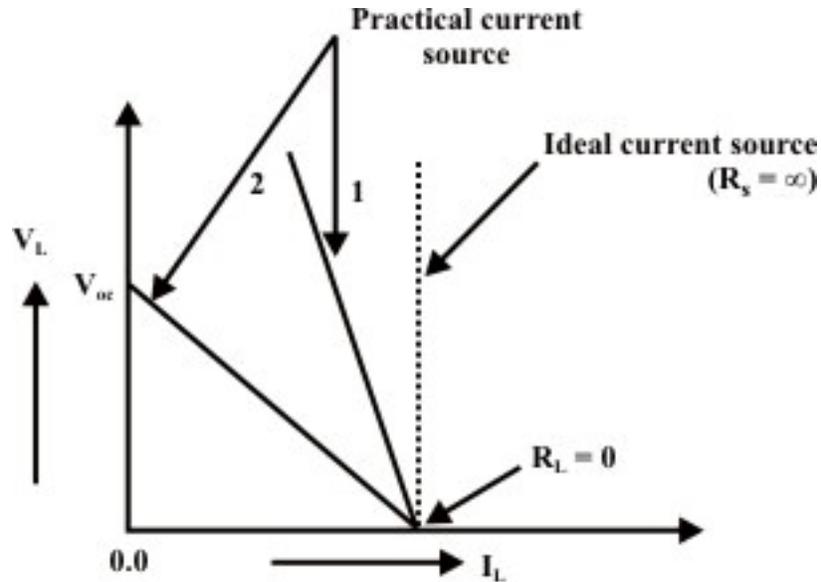


Fig. 3.18: V-I characteristic of practical current source

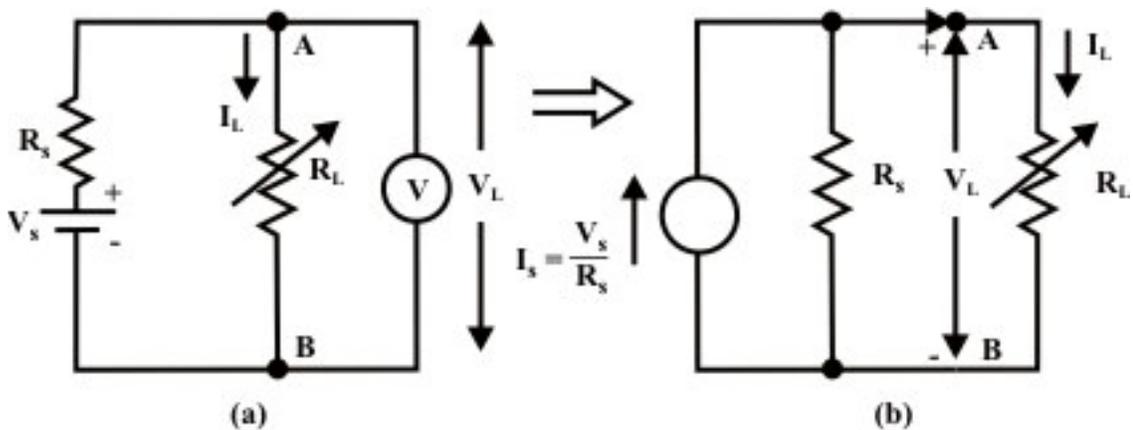


Fig. 3.19: Source Conversions

- Current source to Voltage Source

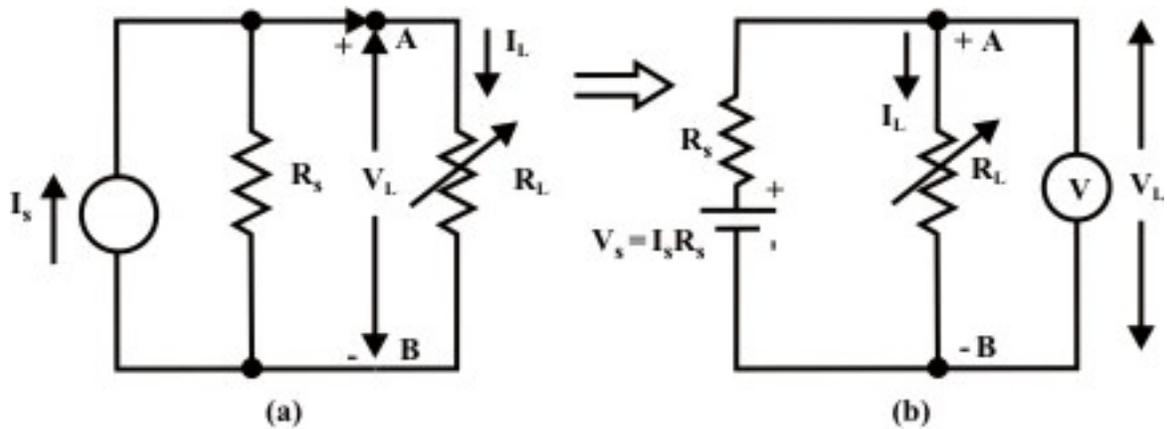


Fig. 3.20: Current Source to Voltage source conversion

For the circuit in fig. 3.15(a), the load voltage V_L is given by

$$V_L = I_L R_L = \left(\frac{R_s}{R_s + R_L} \times I_s \right) R_L = I_s R_s \left(\frac{R_L}{R_s + R_L} \right) = V_s \left(\frac{R_L}{R_s + R_L} \right) \quad (3.5)$$

Equation (3.5) represents output from the voltage source across a load resistance and this act as a voltage divider circuit. Figure 3.20(b) describes the situation that a voltage source with a voltage value $V_s = I_s R_s$ and an internal source resistance R_s has an equivalent effect on the same load resistor as the current source in figure 3.20(a).

Note: A current source with a magnitude of current I_s and a source internal resistance R_s can be replaced by an equivalent voltage source of magnitude $V_s = I_s R_s$ and an internal source resistance R_s (see fig. 3.20(b)).

Remarks on practical sources: (i) The open circuit voltage that appears at the terminals A & B for two sources (voltage & current) is same (i.e., V_s).

(ii) When the terminals A & B are shorted by an ammeter, the short-circuit results same in both cases (i.e., I_s).

(iii) If an arbitrary resistor (R_L) is connected across the output terminals A & B of either source, the same power will be dissipated in it.

(iv) The sources are equivalent only as concerns on their behavior at the external terminals.

(v) The internal behavior of both sources is quite different (i.e., when open circuit the voltage source does not dissipate any internal power while the current source dissipates. Reverse situation is observed in short-circuit condition).

L-3.8 Independent and Dependent Sources that encountered in electric circuits

- Independent Sources

So far the voltage and current sources (whether ideal or practical) that have been discussed are known as independent sources and these sources play an important role

to drive the circuit in order to perform a specific job. The internal values of these sources (either voltage source or current source) – that is, the generated voltage V_s or the generated current I_s (see figs. 3.15 & 3.17) are not affected by the load connected across the source terminals or across any other element that exists elsewhere in the circuit or external to the source.

- Dependent Sources

Another class of electrical sources is characterized by dependent source or controlled source. In fact the source voltage or current depends on a voltage across or a current through some other element elsewhere in the circuit. Sources, which exhibit this dependency, are called dependent sources. Both voltage and current types of sources may be dependent, and either may be controlled by a voltage or a current. In general, dependent source is represented by a diamond (\diamond)-shaped symbol as not to confuse it with an independent source. One can classify dependent voltage and current sources into four types of sources as shown in fig.3.21. These are listed below:

- (i) Voltage-controlled voltage source (VCVS) (ii) Current-controlled voltage source (ICVS)
- (iii) Voltage-controlled current source (VCIS) (iv) Current-controlled current source (ICIS)

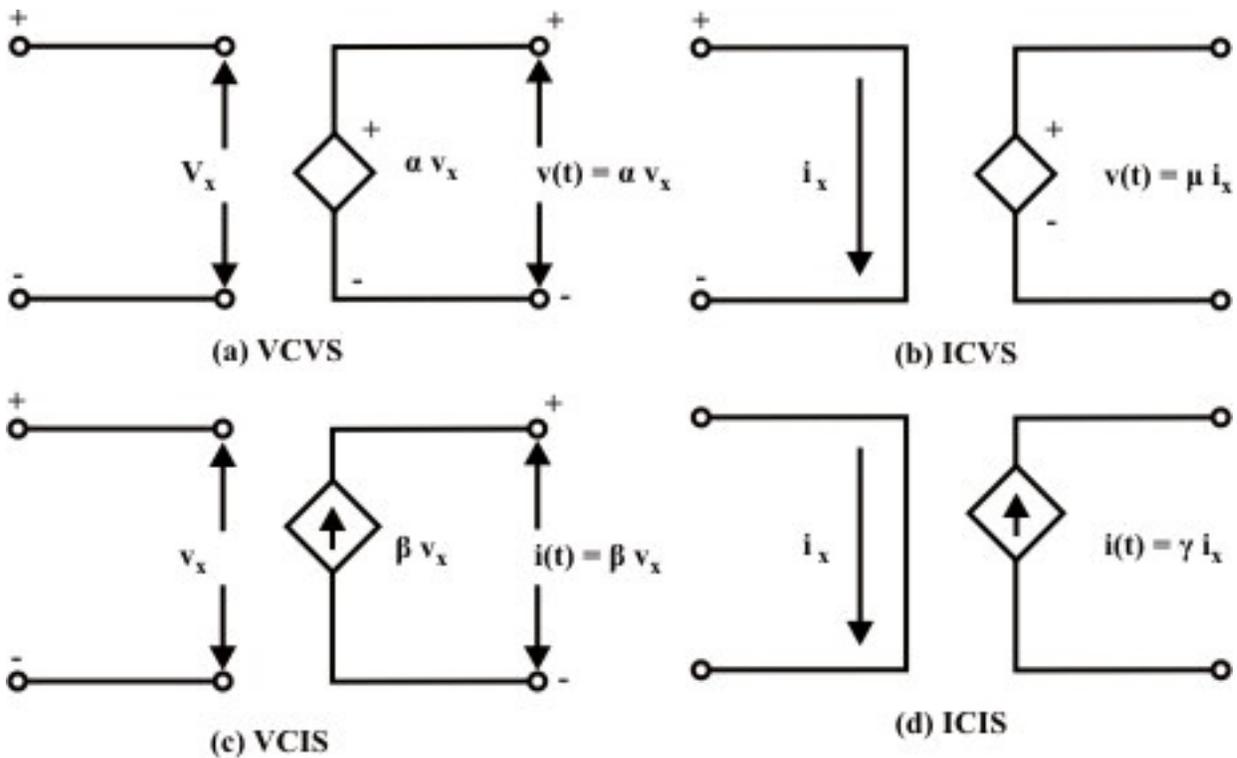


Fig. 3.21: Ideal dependent (controlled) sources

Note: When the value of the source (either voltage or current) is controlled by a voltage (v_x) somewhere else in the circuit, the source is said to be voltage-controlled

source. On the other hand, when the value of the source (either voltage or current) is controlled by a current (i_x) somewhere else in the circuit, the source is said to be current-controlled source. KVL and KCL laws can be applied to networks containing such dependent sources. Source conversions, from dependent voltage source models to dependent current source models, or visa-versa, can be employed as needed to simplify the network. One may come across with the dependent sources in many equivalent-circuit models of electronic devices (transistor, BJT(bipolar junction transistor), FET(field-effect transistor) etc.) and transducers.

L-3.9 Understanding Delivering and Absorbing Power by the Source.

It is essential to differentiate between the absorption of power (or dissipating power) and the generating (or delivering) power. The power absorbed or dissipated by any circuit element when flows in a load element from higher potential point (i.e +ve terminal) toward the lower terminal point (i.e., -ve terminal). This situation is observed when charging a battery or source because the source is absorbing power. On the other hand, when current flows in a source from the lower potential point (i.e., -ve terminal) toward the higher potential point (i.e., +ve terminal), we call that source is generating power or delivering power to the other elements in the electric circuit. In this case, one can note that the battery is acting as a “source” whereas the other element is acting as a “sink”. Fig.3.22 shows mode of current entering in a electric element and it behaves either as source (delivering power) or as a sink (absorbing or dissipating power).

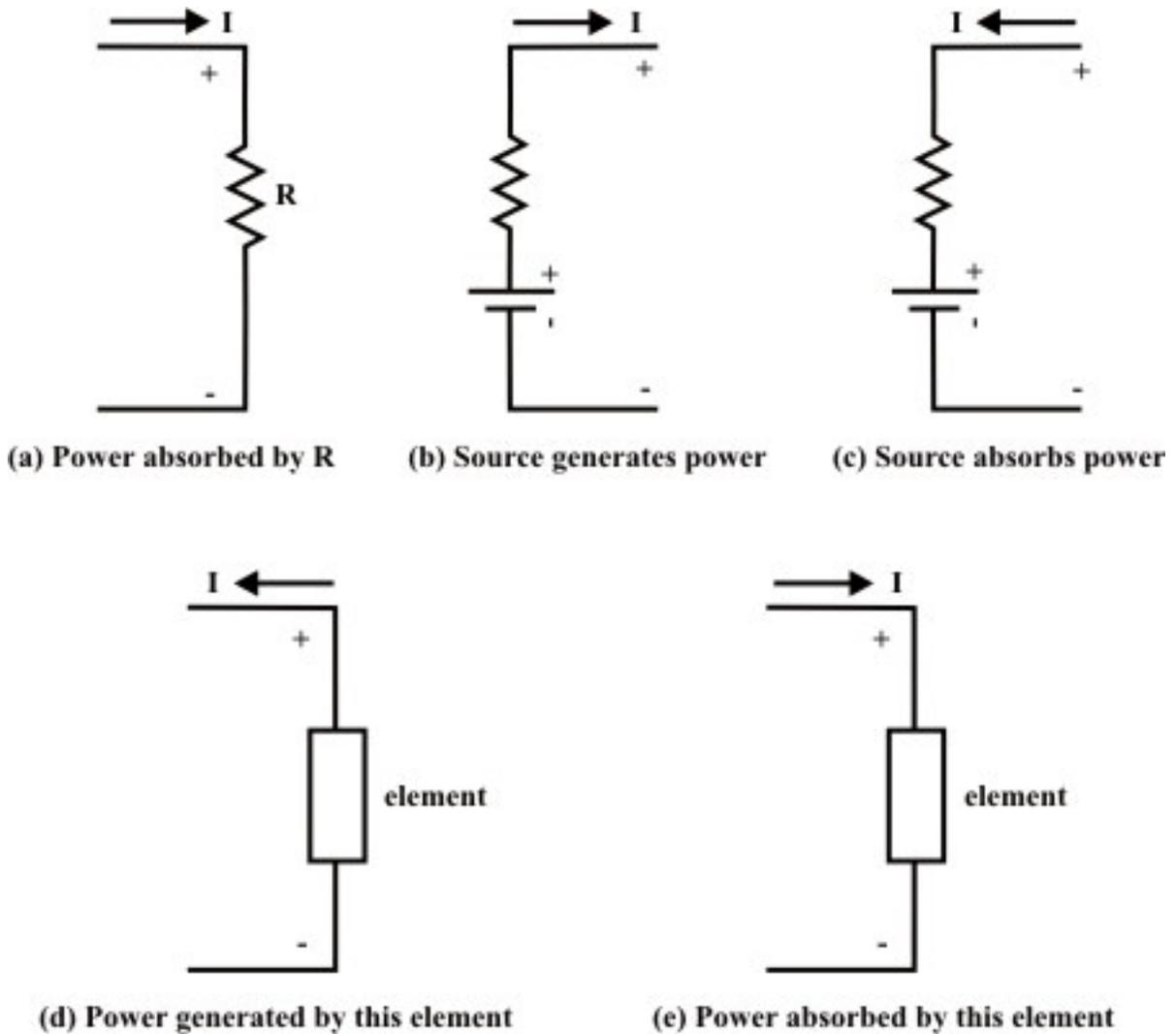


Fig. 3.22: Source and sink configurations

L.3.10 Test Your Understanding [marks distribution shown inside the bracket]

T.1 If a 30 V source can force 1.5 A through a certain linear circuit, how much current can 10 V force through the same circuit? (Ans. 500 mA.) [1]

T.2 Find the source voltage V_s in the circuit given below [1]

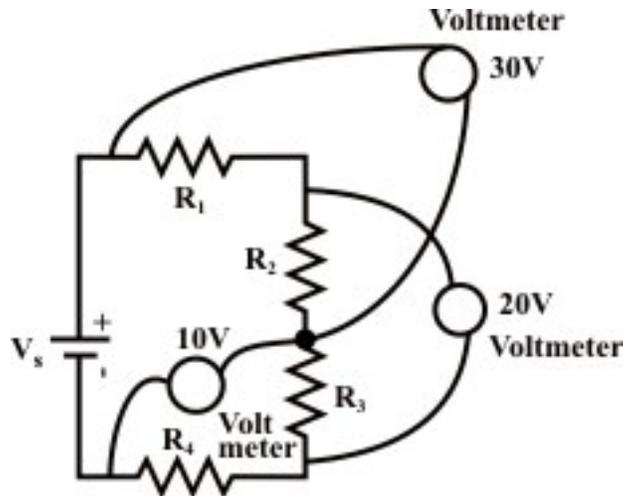


Fig. 3.33

(Ans. 40 V)

T.3 For the circuit shown in Figure T.3

[1x4]

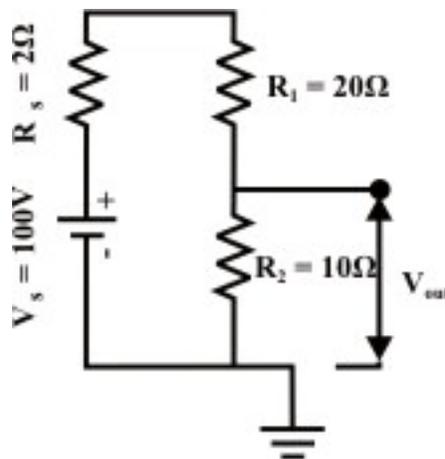


Fig. 3.34

- Calculate V_{out} , ignoring the internal resistance of the source R_s (assuming it's zero). Use Voltage division method. (Ans. 33.333 V)
- Recalculate V_{out} , taking into account R_s . What percentage error was introduced by ignoring R_s in part (a). (Ans. 31.29 V, 6.66%)
- Repeat part (a) & (b) with the same source and replacing $R_1 = 20\Omega$ by $20k\Omega$ & $R_2 = 10\Omega$ by $1k\Omega$. Explain why the percent error is now so much less than in part (b). (Ans. 33.333 V, 33.331 V, 0.006%)

T.4 For the circuit shown in figure T.4

[1x6]

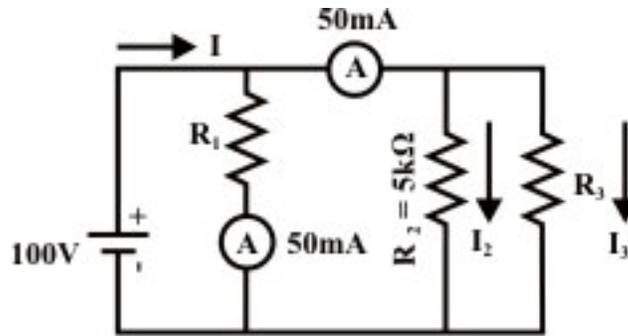


Fig. 3.35

- (a) Find, in any order, I_2 , I_3 , and I (b) Find, in any order, R_1 , R_3 , and R_{eq} .
 (Ans. (a) 20 mA, 30 mA and 100 mA (b) $2\text{ k}\Omega$, $3.33\text{ k}\Omega$ and $1\text{ k}\Omega$.)

T.5 Refer to the circuit shown in Figure T.5

[1x4]

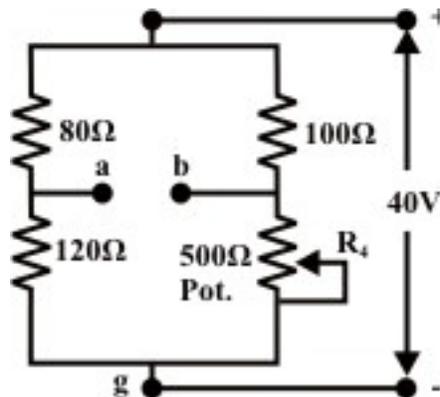


Fig. 3.36

- (a) What value of R_4 will balance the bridge (i.e., $V_{ab} = 0.0$) (b) At balanced condition, find the values of V_{ag} & V_{bg} . (Ans. 150Ω , 24V (a is higher potential than 'g', since current is flowing from 'a' to 'b'), 24V (b is higher potential than 'g'))
- (b) Does the value of V_{ag} depend on whether or not the bridge is balanced? Explain this. (Ans. No., since flowing through the 80Ω branch will remain same and hence potential drop across the resistor remains same.)
- (c) Repeat part (b) for V_{bg} . (Ans. Yes. Suppose the value of R_4 is increased from its balanced condition, this in turn decreases the value of current in that branch and subsequently voltage drop across the 100Ω is also decreases. This indicates that the voltage across V_{bg} will increase to satisfy the KVL.)
- (d) If the source voltage is changed to 50 V will the answer to part (a) change? Explain this. (Ans. No.)

T.6 If an ideal voltage source and an ideal current source are connected in parallel, then the combination has exactly the same properties as a voltage source alone. Justify this statement. [1]

T.7 If an ideal voltage source and an ideal current source are connected in series, the combination has exactly the same properties as a current source alone. Justify this statement. [1]

T.8 When ideal arbitrary voltage sources are connected in parallel, this connection violates KVL. Justify. [1]

T.9 When ideal arbitrary current sources are connected in series, this connection violates KCL. Justify. [1]

T.10 Consider the nonseries-parallel circuit shown in figure T.10. Determine R and the equivalent resistance R_{eq} between the terminals “a” & “b” when $v_1 = 8V$.

(Applying basic two Kirchhoff’s laws) (Ans. $R = 4\Omega$ & $R_{eq} = 4\Omega$) [3]

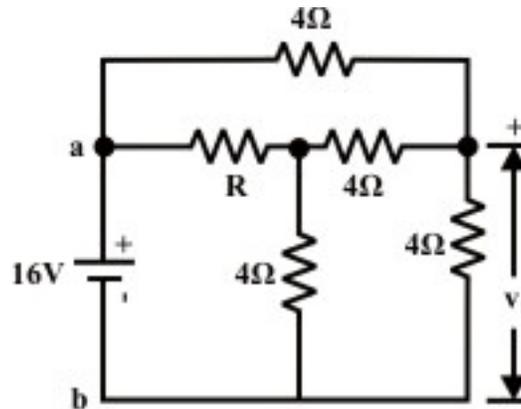


Fig. 3.37

T.11 A 20 V voltage source is connected in series with the two series-resistors $R_1 = 5\Omega$ & $R_2 = 10\Omega$. (a) Find I , V_{R1} , V_{R2} . (Ans. 1.333 A, 6.6667 V, 13.33 V)

(b) Find the power absorbed or generated by each of the three elements. (8.88 W (absorbed), 17.76 W (absorbed), 26.66 W delivered or generated (since current is leaving the plus terminal of that source.)) [2]

T.12 Consider the circuit of figure T.12

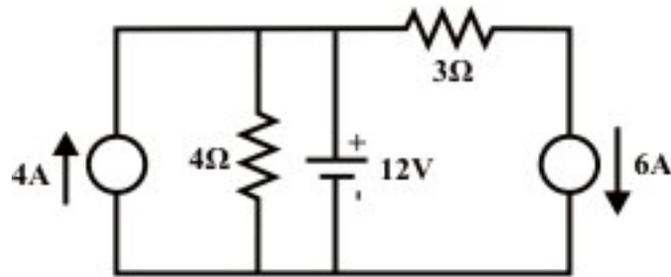


Fig. 3.38

Find powers involved in each of the five elements and whether absorbed or generated. (Ans. 48 W (G), 36 W (A), 60 W (G), 108 W (A) and 36 W (G). (results correspond to elements from left to right, CS, R, VS, R, CS). [4]

T.13 For the circuit of Figure T.13 Suppose $V_{in} = 20V$.

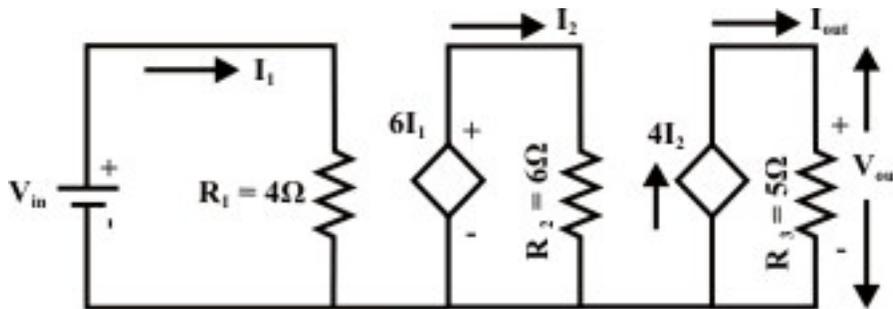


Fig. 3.39

(a) Find the output voltage and output current. [2]

(b) Find the ratio of output voltage (V_{out}) to input voltage (V_{in}) i.e. $\frac{V_{out}}{V_{in}} =$ voltage gain. [1]

(c) Find the power delivered by each source(dependent & independent sources).[2]

(Ans. (a) 100 V, 20 A (note that $6I_1$ is the value of dependent voltage source with the polarity as shown in fig. T.13 whereas $4I_2$ represents the value of dependent current source) (b) 5 (voltage gain). (c) 100 W (VS), 150 W (DVS), 2000 W (DCS)).

T.14 Find the choice of the resistance R_2 (refer to Fig. T.13) so that the voltage gain is 30. (Ans. $R_2 = 1\Omega$) [1]

T.15 Find equivalent resistance between the terminals 'a' & 'b' and assume all resistors values are 1Ω . [2]

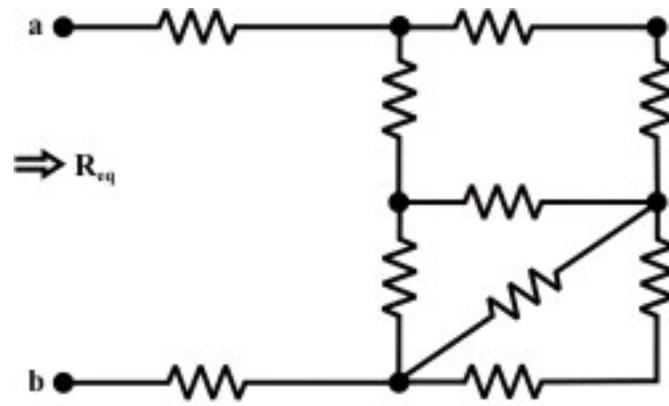


Fig. 3.40

Module 2 DC Circuit

Lesson

4

Loop Analysis of resistive circuit in the context of dc voltages and currents

Objectives

- Meaning of circuit analysis; distinguish between the terms mesh and loop.
- To provide more general and powerful circuit analysis tool based on Kirchhoff's voltage law (KVL) only.

L.4.1 Introduction

The Series-parallel reduction technique that we learned in lesson-3 for analyzing DC circuits simplifies every step logically from the preceding step and leads on logically to the next step. Unfortunately, if the circuit is complicated, this method (the simplify and reconstruct) becomes mathematically laborious, time consuming and likely to produce mistake in calculations. In fact, to elevate these difficulties, some methods are available which do not require much thought at all and we need only to follow a well-defined faithful procedure. One most popular technique will be discussed in this lesson is known as 'mesh or loop' analysis method that based on the fundamental principles of circuits laws, namely, Ohm's law and Kirchhoff's voltage law. Some simple circuit problems will be analyzed by hand calculation to understand the procedure that involve in mesh or loop current analysis.

L.4.1.1 Meaning of circuit analysis

The method by which one can determine a variable (either a voltage or a current) of a circuit is called analysis. Basic difference between 'mesh' and 'loop' is discussed in lesson-3 with an example. A 'mesh' is any closed path in a given circuit that does not have any element (or branch) inside it. A mesh has the properties that (i) every node in the closed path is exactly formed with two branches (ii) no other branches are enclosed by the closed path. Meshes can be thought of a resembling window partitions. On the other hand, 'loop' is also a closed path but inside the closed path there may be one or more than one branches or elements.

L.4.2 Solution of Electric Circuit Based on Mesh (Loop) Current Method

Let us consider a simple dc network as shown in Figure 4.1 to find the currents through different branches using Mesh (Loop) current method.

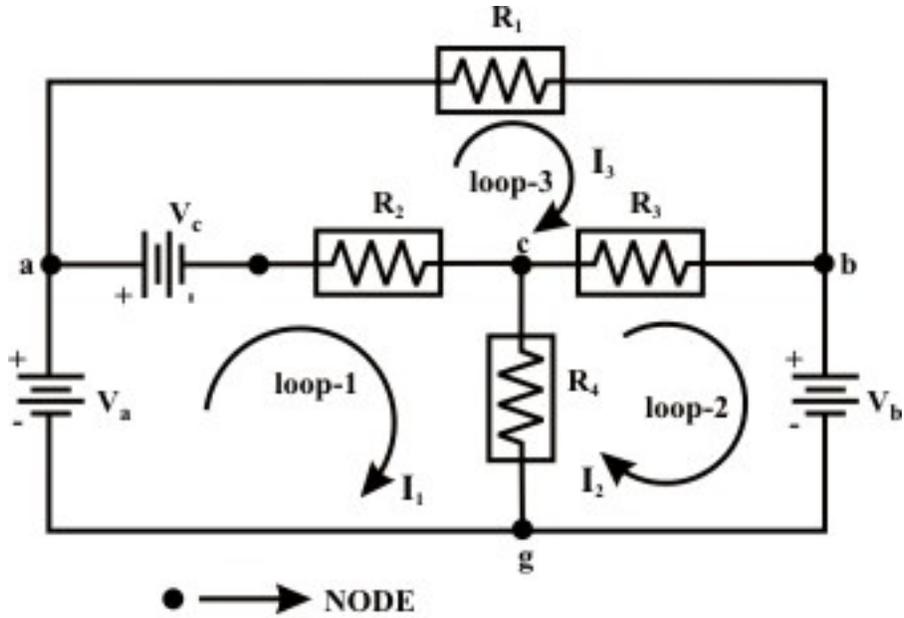


Figure 4.1

Applying KVL around mesh (loop)-1:(note in mesh-1, I_1 is known as local current and other mesh currents I_2 & I_3 are known as foreign currents.)

$$V_a - V_c - (I_1 - I_3)R_2 - (I_1 - I_2)R_4 = 0$$

$$V_a - V_c = (R_2 + R_4)I_1 - R_4I_2 - R_2I_3 = R_{11}I_1 - R_{12}I_2 - R_{13}I_3 \quad (4.1)$$

Applying KVL around mesh (loop)-2:(similarly in mesh-2, I_2 is local current and I_1 & I_3 are known as foreign currents)

$$-V_b - (I_2 - I_3)R_3 - (I_2 - I_1)R_4 = 0$$

$$-V_b = -R_4I_1 + (R_3 + R_4)I_2 - R_3I_3 = -R_{21}I_1 + R_{22}I_2 - R_{23}I_3 \quad (4.2)$$

Applying KVL around mesh (loop)-3:

$$V_c - I_3R_1 - (I_3 - I_2)R_3 - (I_3 - I_1)R_2 = 0$$

$$V_c = -R_2I_1 - R_3I_2 + (R_1 + R_2 + R_3)I_3 = -R_{31}I_1 - R_{32}I_2 + R_{33}I_3 \quad (4.3)$$

** In general, we can write for i^{th} mesh (for $i = 1, 2, \dots, N$)

$$\sum V_{ii} = -R_{i1}I_1 - R_{i2}I_2 \dots \dots \dots + R_{ii}I_i - R_{i,i+1}I_{i+1} - \dots - R_{iN}I_N$$

$\sum V_{ii} \rightarrow$ simply means to take the algebraic sum of all voltage sources around the i^{th} mesh.

$R_{ii} \rightarrow$ means the total self resistance around the i^{th} mesh.

$R_{ij} \rightarrow$ means the mutual resistance between the and j^{th} meshes.

Note: Generally, $R_{ij} = R_{ji}$ (true only for linear bilateral circuits)

$I_i \rightarrow$ the unknown mesh currents for the network.

Summarize:

Step-1: Draw the circuit on a flat surface with no conductor crossovers.

Step-2: Label the mesh currents (I_i) carefully in a clockwise direction.

Step-3: Write the mesh equations by inspecting the circuit (No. of independent mesh (loop) equations=no. of branches (b) - no. of principle nodes (n) + 1).

Note:

To analysis, a resistive network containing voltage and current sources using 'mesh' equations method the following steps are essential to note:

- If possible, convert current source to voltage source.
- Otherwise, define **the voltage** across the current source and write the mesh equations as if these source voltages were known. Augment the set of equations with one equation for each current source expressing a known mesh current or difference between two mesh currents.
- Mesh analysis is valid only for circuits that can be drawn in a two-dimensional plane in such a way that no element crosses over another.

Example-L-4.1: Find the **current** through 'ab-branch' (I_{ab}) and **voltage** (V_{cg}) across the current source using Mesh-current method.

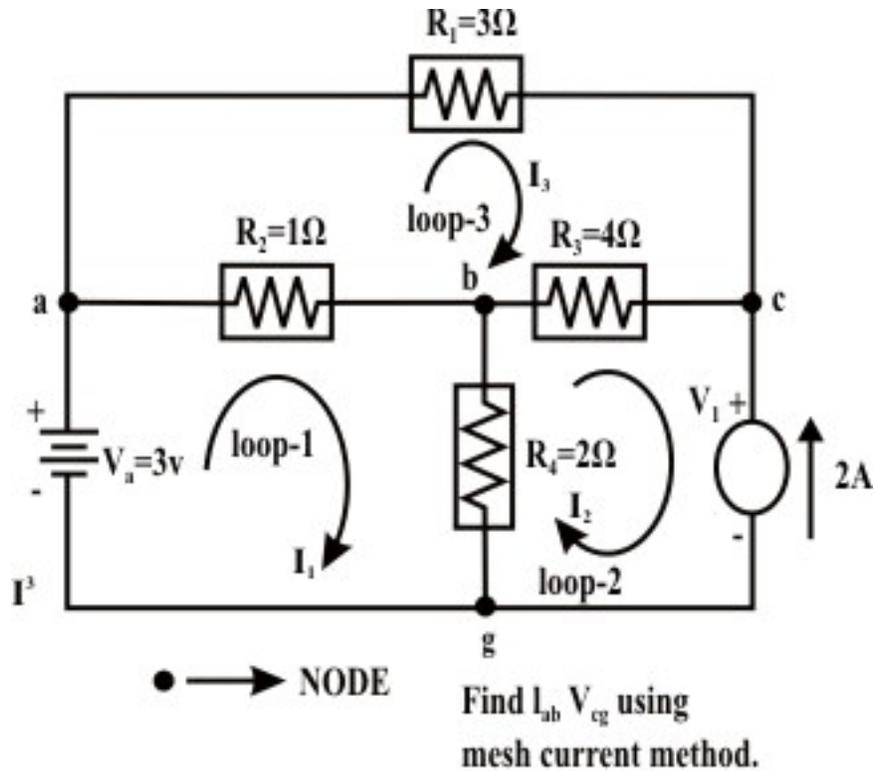


Figure 4.2

Solution: Assume voltage across the current source is v_1 ('c' is higher potential than 'g' (ground potential and assumed as zero potential) and note $I_2 = -2A$ (since assigned current direction (I_2) is opposite to the source current)

Loop - 1: (Applying KVL)

$$\begin{aligned}
 V_a - (I_1 - I_3)R_2 - (I_1 - I_2)R_4 &= 0 \Rightarrow 3 = 3I_1 - 2I_2 - I_3 \\
 3I_1 - I_3 &= -1
 \end{aligned}
 \tag{4.4}$$

Loop - 2: (Applying KVL)

Let us assume the voltage across the current source is v_1 and its top end is assigned with a positive sign.

$$\begin{aligned}
 -v_1 - (I_2 - I_1)R_4 - (I_2 - I_3)R_3 &= 0 \Rightarrow -v_1 = -2I_1 + 6I_2 - 4I_3 \\
 2I_1 + 12 + 4I_3 &= v_1 \quad (\text{note: } I_2 = -2A)
 \end{aligned}
 \tag{4.5}$$

Loop - 3: (Applying KVL)

$$\begin{aligned}
 -I_3 R_1 - (I_3 - I_2)R_3 - (I_3 - I_1)R_2 &= 0 \Rightarrow -I_1 - 4I_2 + 8I_3 = 0 \\
 I_1 - 8I_3 &= 8 \quad (\text{Note, } I_2 = -2A)
 \end{aligned}
 \tag{4.6}$$

Solving equations (4.4) and (4.6), we get $I_1 = -\frac{48}{69} = -0.6956A$ and

$$I_3 = -\frac{25}{23} = -1.0869A, \quad I_{ab} = I_1 - I_3 = 0.39A, \quad I_{bc} = I_2 - I_3 = -0.913A \quad \text{and}$$

$$I_{bg} = I_1 - I_2 = 1.304A$$

- ve sign of current means that the current flows in reverse direction (in our case, the current flows through 4Ω resistor from 'c' to 'b' point). From equation (4.5), one can get $v_1 = 6.27$ volt.

Another way: $-v_1 + v_{bg} + v_{bc} = 0 \Rightarrow v_1 = v_{cg} = 6.27$ volt.

Example-L-4.2 For the circuit shown Figure 4.3 (a) find V_x using the mesh current method.

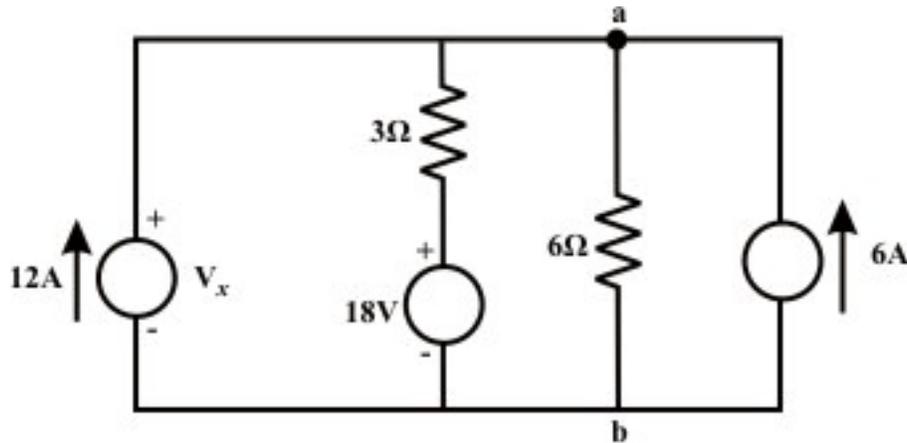


Fig. 4.3(a)

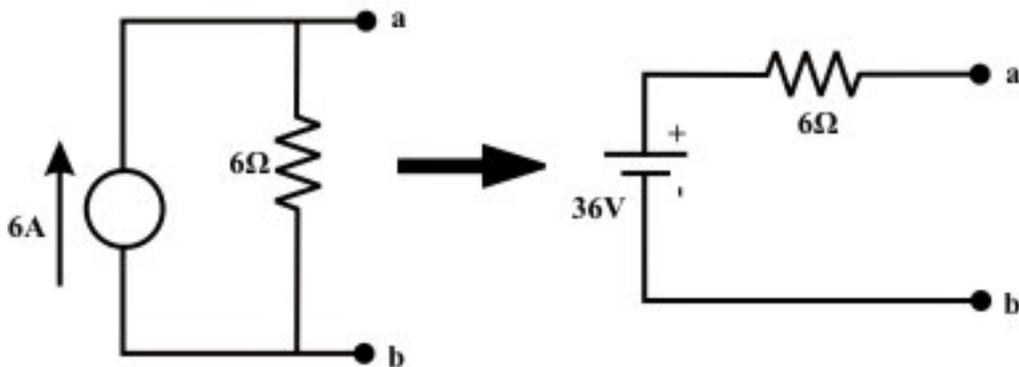


Fig. 4.3(b)

Solution: One can easily convert the extreme right current source (6 A) into a voltage source. Note that the current source magnitude is 6 A and its internal resistance is 6Ω . The given circuit is redrawn and shown in Figure 4.3 (c)

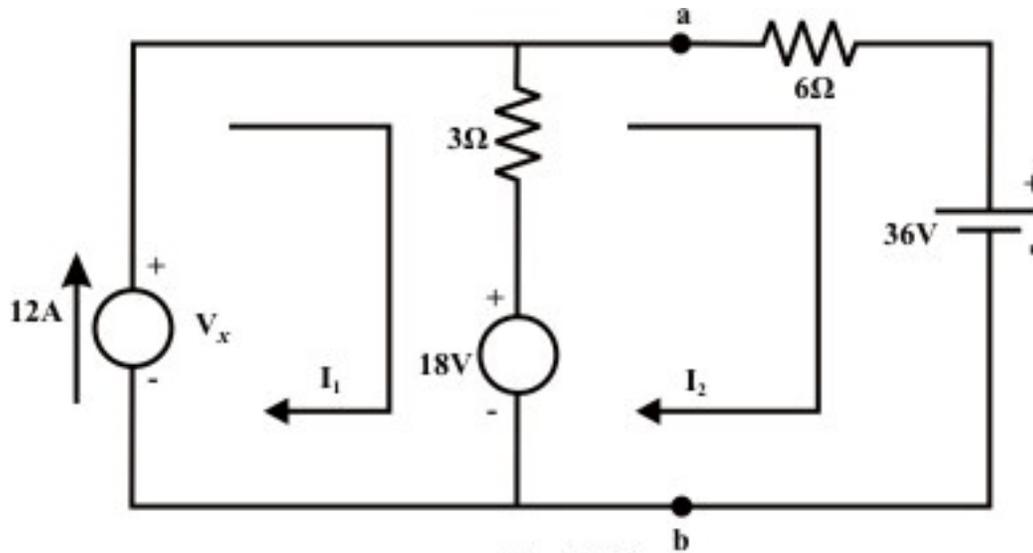


Fig. 4.3(c)

Loop-1: (Write KVL, note $I_1 = 12 A$)

$$V_x - (I_1 - I_2) \times 3 - 18 = 0 \Rightarrow V_x + 3I_2 = 54 \quad (4.7)$$

Loop-2: (write KVL)

$$18 - (I_2 - I_1) \times 3 - I_2 \times 6 - 36 = 0 \Rightarrow 9I_2 = 18 \Rightarrow I_2 = 2 A$$

Using the value of $I_2 = 2 A$ in equation (4.7), we get $V_x = 48 \text{ volt}$.

Example-L-4.3 Find v_R for the circuit shown in figure 4.4 using ‘mesh current method’. Calculate the power absorbed or delivered by the sources and all the elements.

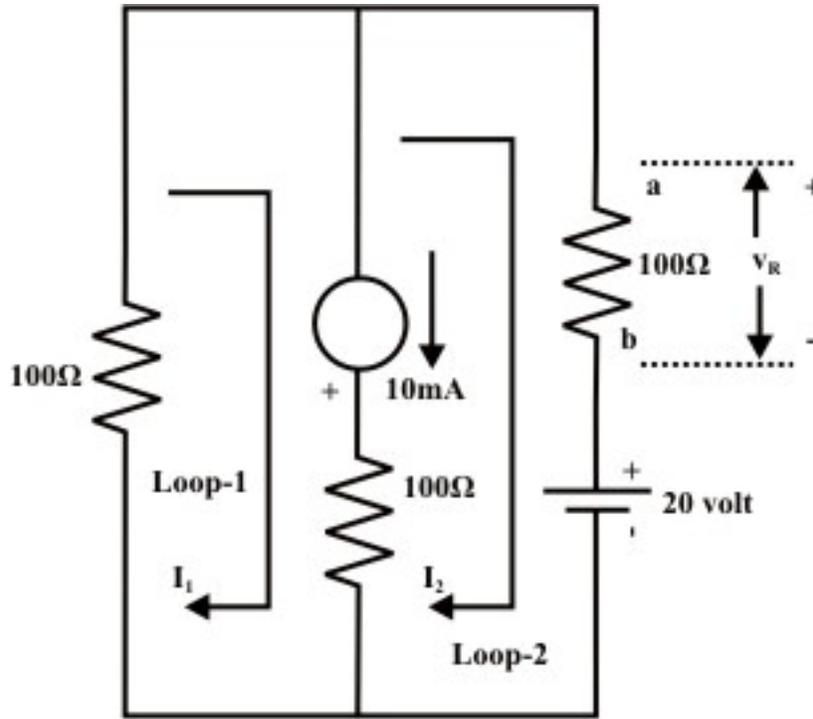


Figure 4.4

Solution: Assume the voltage across the current source is ‘ v ’ and the bottom end of current source is marked as positive sign.

For loop No. 1: (KVL equation)

$$v - (I_1 - I_2) \times 100 - I_1 \times 100 = 0 \Rightarrow v - 200I_1 + 100I_2 = 0 \quad (4.8)$$

It may be noted that from the figure that the current flowing through the 100Ω resistor (in the middle branch) is 10mA . More specifically, one can write the following expression

$$I_1 - I_2 = 10 \times 10^{-3} \quad (4.9)$$

For loop No. 2: (KVL equation)

$$-20 - (I_2 - I_1) \times 100 - v - I_2 \times 100 = 0 \Rightarrow v + 200I_2 - 100I_1 = -20 \quad (4.10)$$

Solving equations (4.8)–(4.10), one can obtain the loop currents as $I_1 = -0.095 = -95\text{mA}$ (-ve sign indicates that the assigned loop current direction is not correct or in other words loop current (I_1) direction is anticlockwise.) and $I_2 = -0.105 = -105\text{mA}$ (note, loop current (I_2) direction is anticlockwise). Now the voltage across the 100Ω resistor (extreme right branch) is given by $v_R = I_2 \times 100 = -0.105 \times 100 = -10.5\text{volt}$. This indicates that the resistor terminal (b) adjacent to the voltage source is more positive than the other end of the resistor terminal

(a). From equation (4.8) $v = -8.5 \text{ volt}$ and this implies that the 'top' end of the current source is more positive than the bottom 'end'.

Power delivered by the voltage source = $20 \times 0.105 = 2.1 \text{ W}$ (note that the current is leaving the positive terminal of the voltage source). On the other hand, the power received or absorbed by the current source = $8.5 \times 0.01 = 0.085 \text{ W}$ (since current entering to the positive terminal (top terminal) of the current source). Power absorbed by the all resistance is given

$$= (0.105)^2 \times 100 + (0.095)^2 \times 100 + (10 \times 10^{-3})^2 \times 100 = 2.015 \text{ W} .$$

Further one can note that the power delivered ($P_d = 2.1 \text{ W}$) = power absorbed ($P_{ab} = 0.085 + 2.015 = 2.1 \text{ W}$) = 2.1 W

L.4.3 Test Your Understanding

[Marks:50]

T.4.1 To write the Kirchhoff's voltage law equation for a loop, we proceed clockwise around the loop, considering voltage rises into the loop equation as ----- terms and voltage drops as ----- terms. [2]

T.4.2 When writing the Kirchhoff's voltage law equation for a loop, how do we handle the situation when an ideal current source is present around the loop? [2]

T.4.3 When a loop current emerges with a positive value from mathematical solution of the system of equations, what does it mean? What does it mean when a loop current emerges with a negative value? [2]

T.4.4 In mesh current method, the current flowing through a resistor can be computed with the knowledge of ----- loop current and ----- loop current. [2]

T.4.5 Find the current through 6Ω resistor for the circuit Figure 4.5 using 'mesh current' method and hence calculate the voltage across the current source. [10]

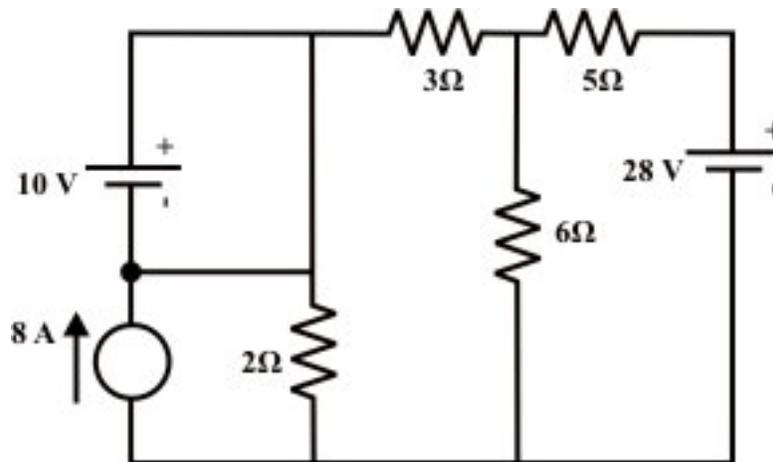


Figure 4.5

(Answer: 3.18 A ; 13.22 V)

T.4.6 For the circuit shown in Figure 4.6, find the current through I_{AB} , I_{AC} , I_{CD} and I_{EF} using ‘mesh current’ method. [12]

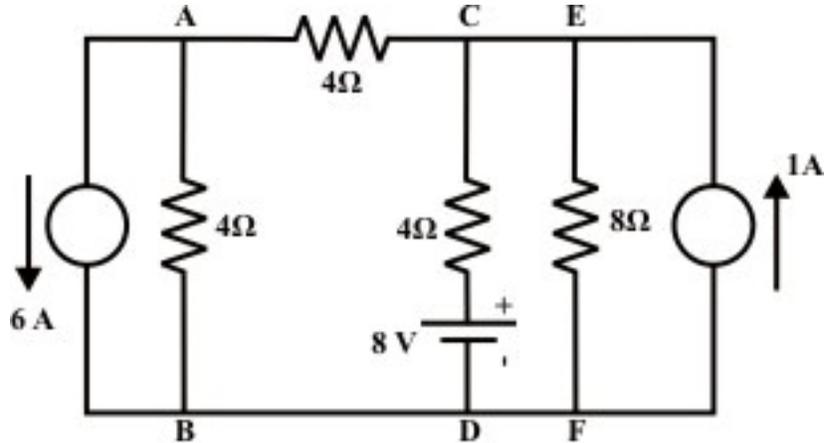


Figure 4.6

(Answer: $I_{AB} = -3\text{ A}$; $I_{AC} = -3\text{ A}$; $I_{CD} = -2\text{ A}$ and $I_{EF} = 0\text{ A}$.)

T.4.7 Find the current flowing through the $R_L = 1\text{ k}\Omega$ resistor for the circuit shown in Figure 4.7 using ‘mesh current’ method. What is the power delivered or absorbed by the independent current source? [10]

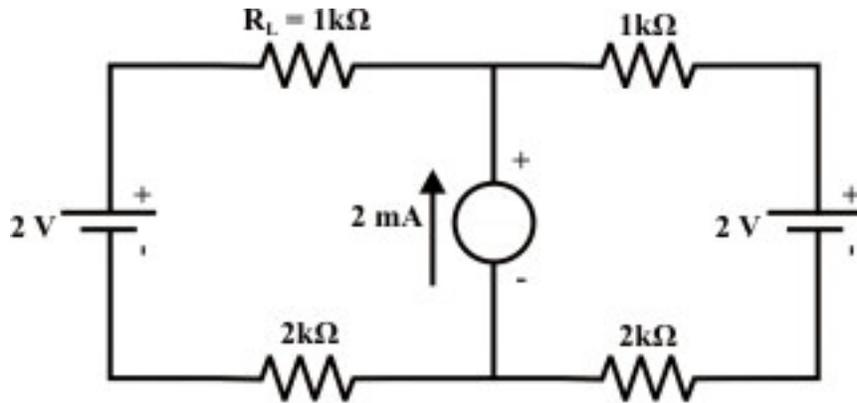


Figure 4.7

(Answer: 1 mA ; 10 mW)

T.4.8 Using ‘mesh current’ method, find the current flowing through 2Ω resistor for the circuit shown in Figure 4.8 and hence compute the power consumed by the same 2Ω resistor. [10]

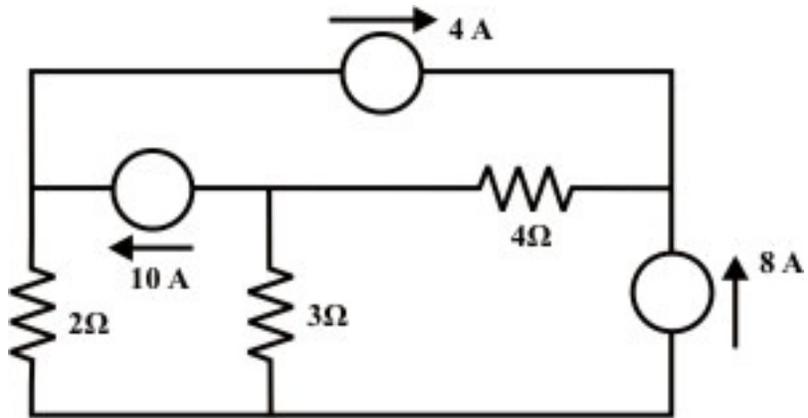


Figure 4.8

(Answer: 6 A; 72W)
